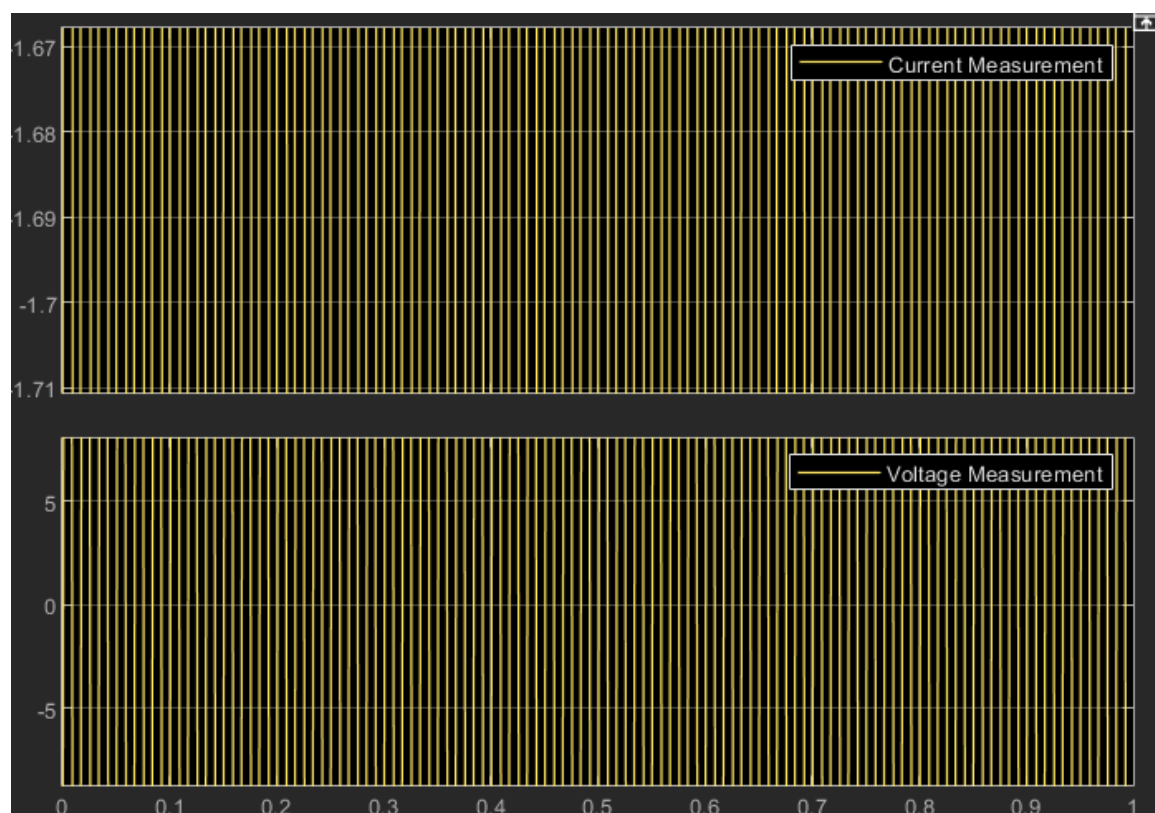*Name: Laila Usama*
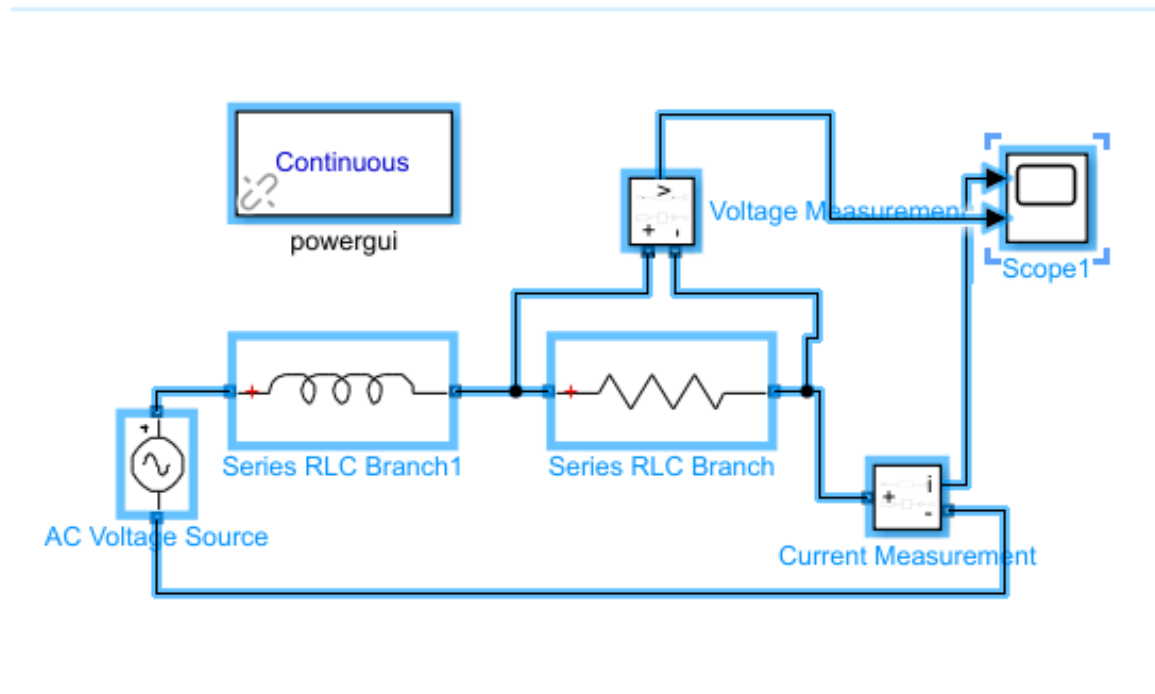
Email: 2100673@eng.asu.edu.eg
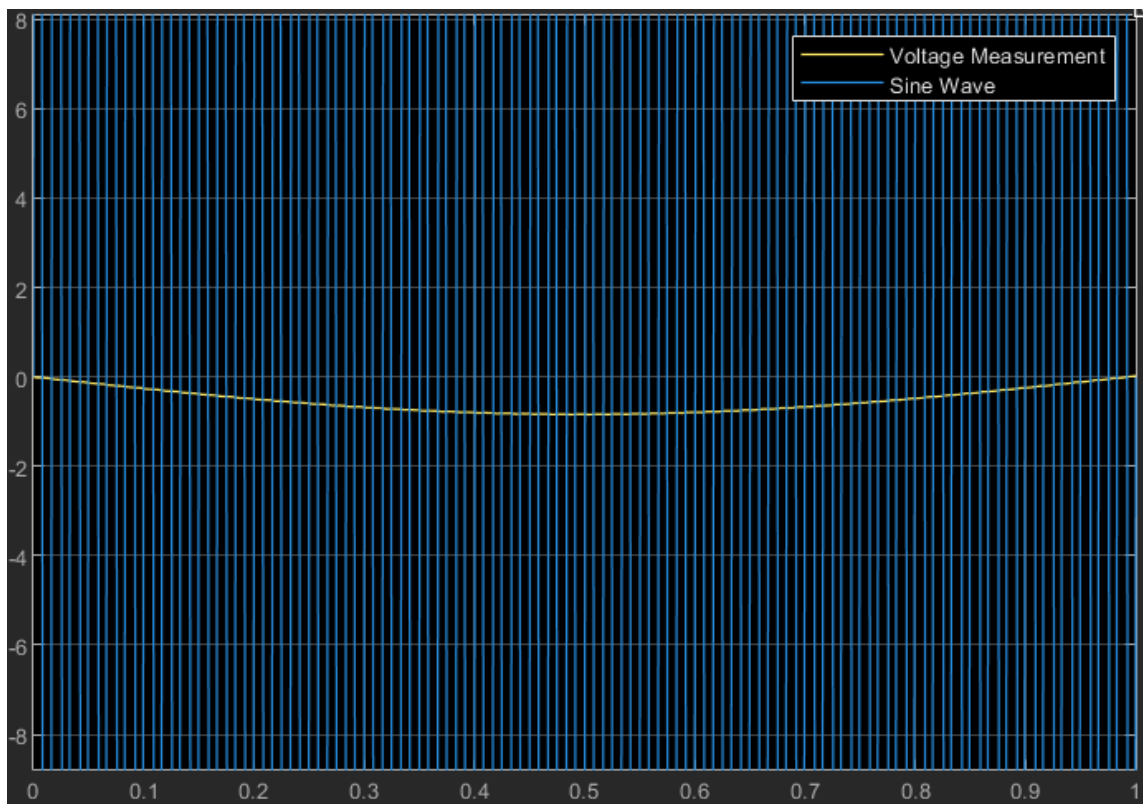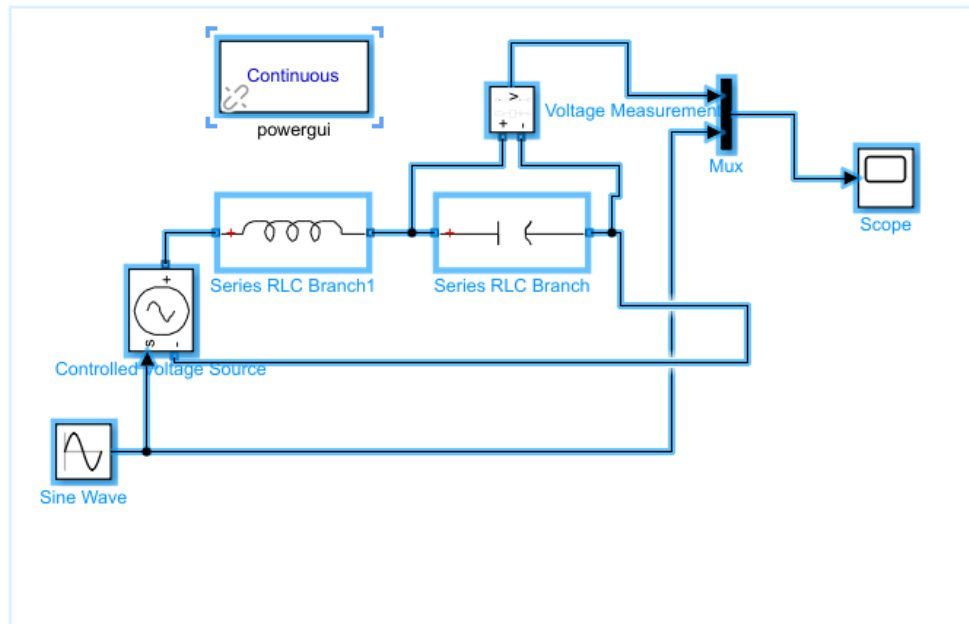
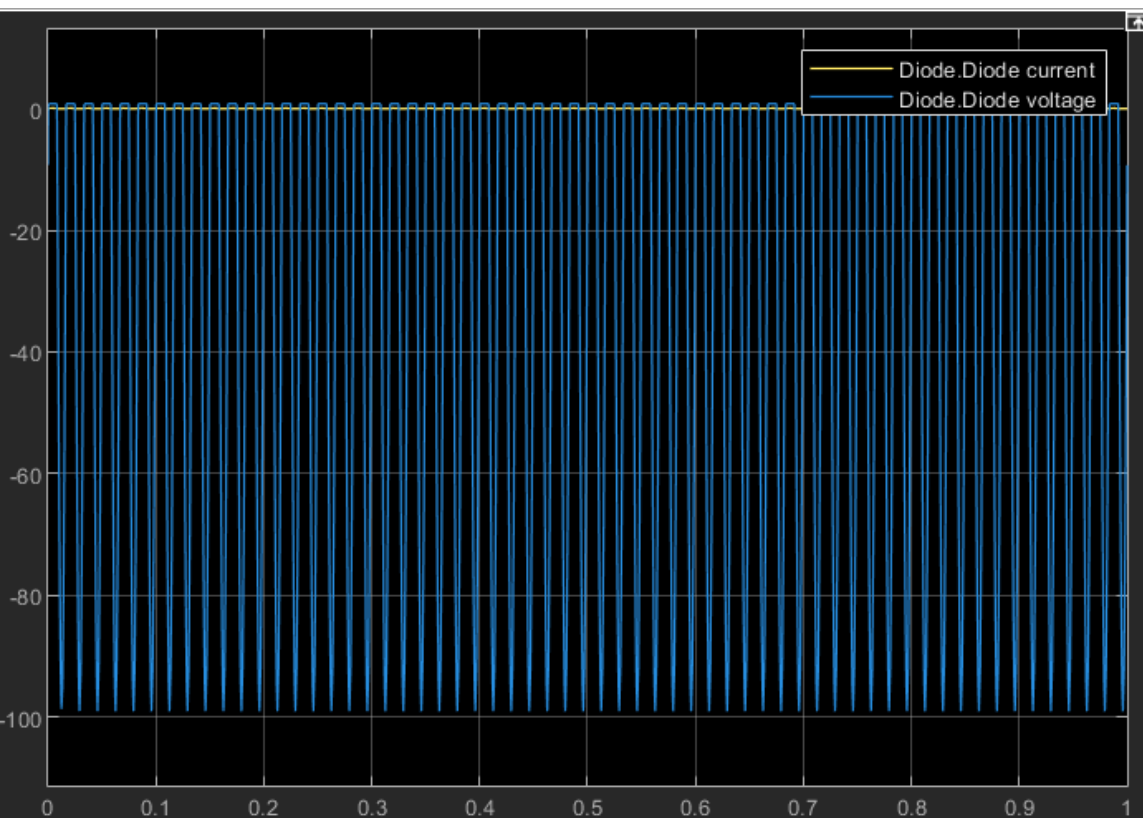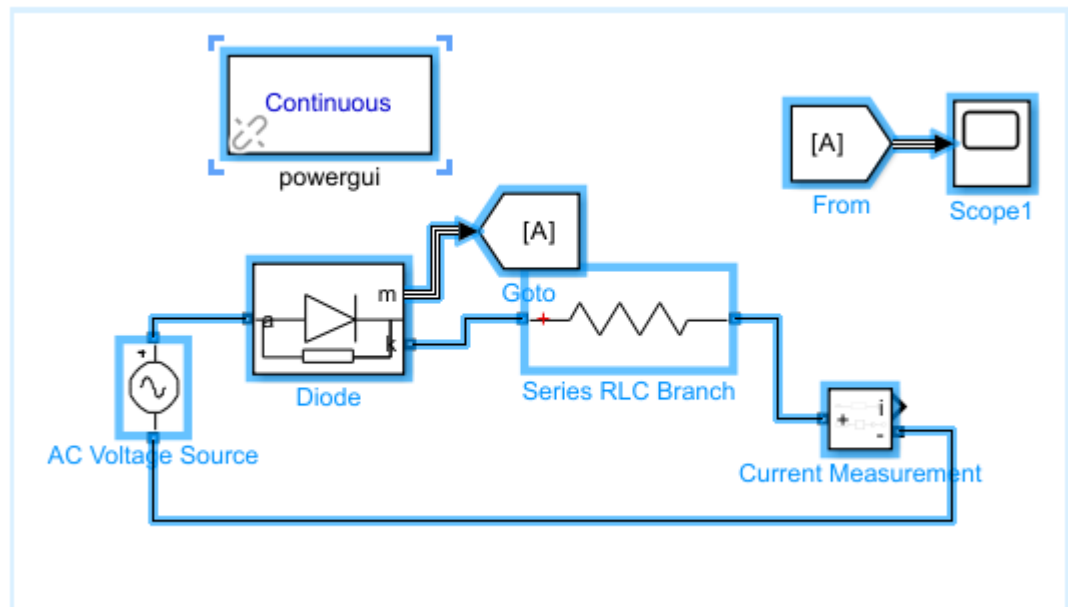*Aviation MATLAB workshop '24*

Session 6

First circuit simulation using Simulink:

Second circuit :

Third circuit:

Zoom in: